

Basic Processor Implementation

Jinyang Li

What we've learnt so far

- Combinatorial logic
 - Truth table
 - ROM
- ALU
- Sequential logic
 - Clocks
 - Basic state elements (SR latch, D latch, flip-flop)



unclocked

Clocked
(Level
triggered)

Clocked
(edge
triggered)

Today's lesson plan

- Implement a basic CPU

Our CPU will be based on RISC-V instead of x86

- 3 popular ISAs now

	ISA	Key advantage	Who builds the processors?	Where are the processors used?
CISC Complex Instruction Set	x86	Fast	Intel, AMD	Server (Cloud), Desktop, Laptop, Xbox console
	ARM	Low power (everybody can license the design from ARM Holdings for \$\$\$)	Samsung, NVIDIA, Qualcomm, Broadcom, Huawei/HiSilicon	Phones, Tablets, Nintendo console, Raspberry Pi
RISC Reduced Instruction Set	RISC-V	Open source, royalty-free	Western digital, Alibaba	Devices (e.g. SSD controllers)

RISC-V at a high level

	RISC-V	X86-64
similarities { # of registers	32	16
Memory	Byte-addressable, Little Endian	Byte-addressable, Little Endian


Why RISC-V is much simpler?

Fewer instructions	50+ (200 manual pages)	1000+ (2306 manual pages)
Simpler instruction encoding	4-byte	Variable length
Simpler instructions	<ul style="list-style-type: none">Ld/st instructions load/store memory to or from registerOther instructions take only register operands	<ul style="list-style-type: none">Instructions take either memory or register operandsComplex memory addressing modes D(B, I, S)Prefixes modify instruction behavior

Basic RISC-V instructions

Registers: x0, x1, x2,..., x31

64-bit

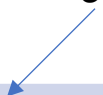

Data transfer	load doubleword	ld x5, 40(x6)	x5=Memory[x6+40]
	store doubleword	sd x5, 40(x6)	Memory[x6+40]=x5
Arithmetic Logical	addition	add x5, x6, x7	x5 = x6 + x7
	subtraction	sub x5, x6, x7	x5 = x6 - x7
	bitwise and	and x5, x6, x7	x5 = x6 & x7
	bitwise or	or x5, x6, x7	x5 = x6 x7
Conditional Branch	Branch if equal	beq x5, x6, 100	If (x5==x6) go to PC+100

RISC-V instruction formats

- All instructions are 32-bit long
 - Several formats encoding operation code (opcode), register numbers ...


Name (Field Size)	Field						Comments
	7 bits	5 bits	5 bits	3 bits	5 bits	7 bits	
R-type	funct7	rs2	rs1	funct3	rd	opcode	Arithmetic instruction format
I-type	immediate[11:0]		rs1	funct3	rd	opcode	Loads & immediate arithmetic
S-type	immed[11:5]	rs2	rs1	funct3	immed[4:0]	opcode	Stores
SB-type	immed[12,10:5]	rs2	rs1	funct3	immed[4:1,11]	opcode	Conditional branch format
UJ-type	immediate[20,10:1,11,19:12]				rd	opcode	Unconditional jump format
U-type	immediate[31:12]				rd	opcode	Upper immediate format

Opcode determines type of instruction

R-type: arithmetic logic instructions

Example R-type instruction:

```
add x5, x6, x7 // x5=x6+x7
```

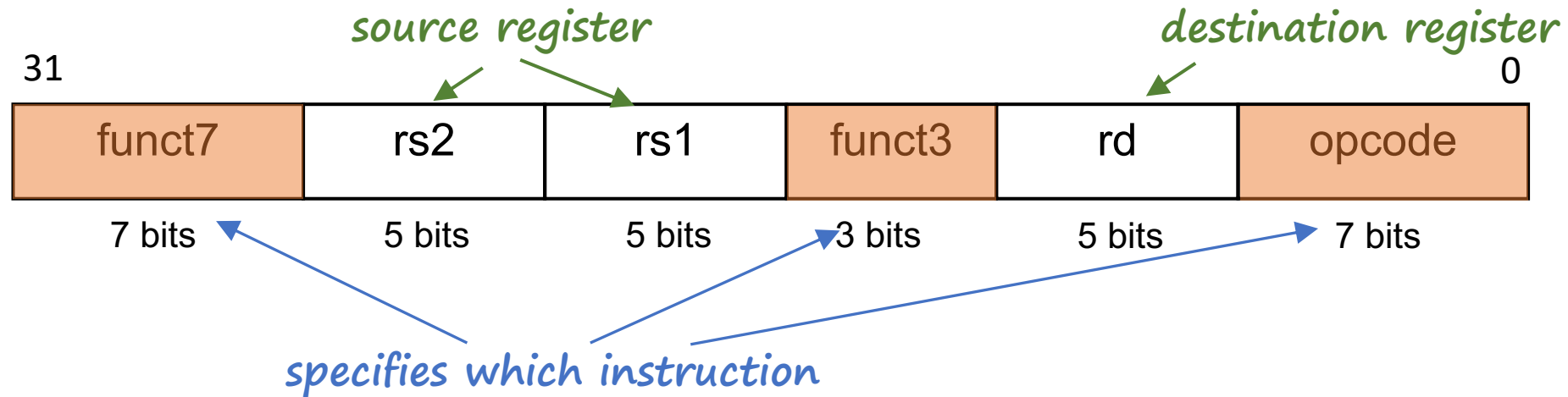


	opcode	funct3	funct7
add	0110011	000	0000000
sub	0110011	000	0100000
xor	0110011	100	0000000

I-type: loads and immediate arithmetic

Example I-type instruction:

```
ld x5, 40(x6) //x5=Memory[x6+40]
```

```
addi x5, x6, 100 // x5=x6+100
```

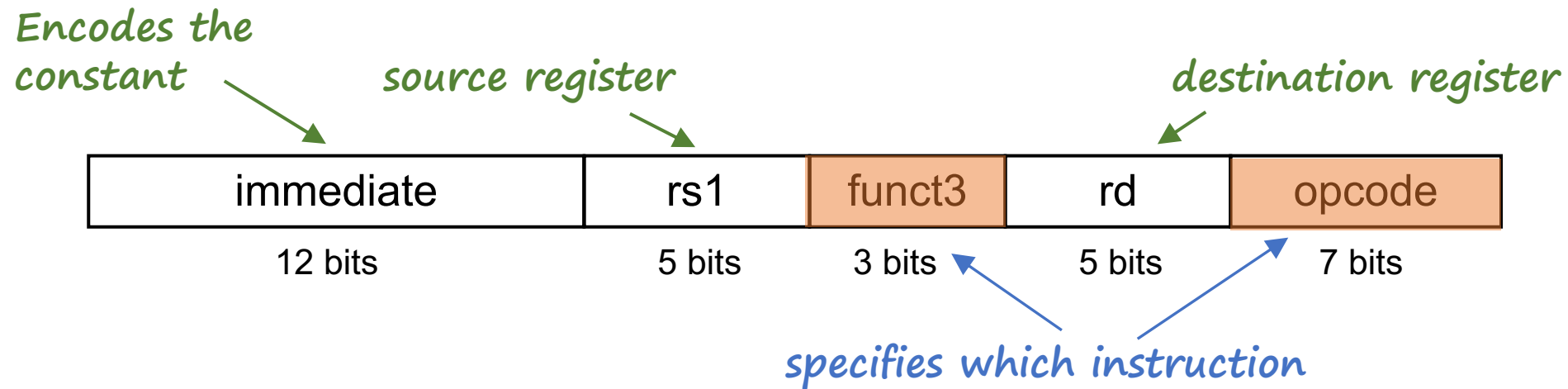


	opcode	funct3
ld	0000011	011
addi (add immediate)	0010011	000

S-type: stores

Example S-type instruction:

```
sd x5, 40(x6) //Memory[x6+40]=x5
```

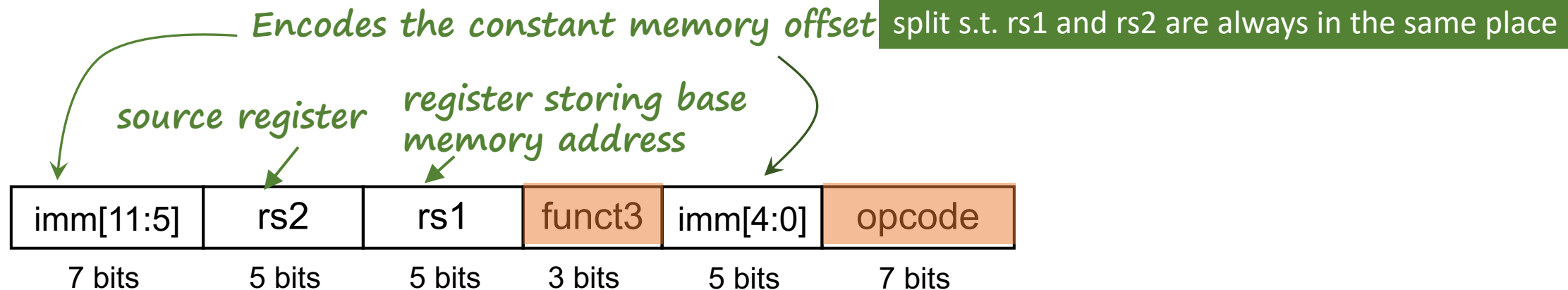


	opcode	funct3
sw (store word)	0100011	010
sd (store doubleword)	0100011	111

SB-type: conditional branch

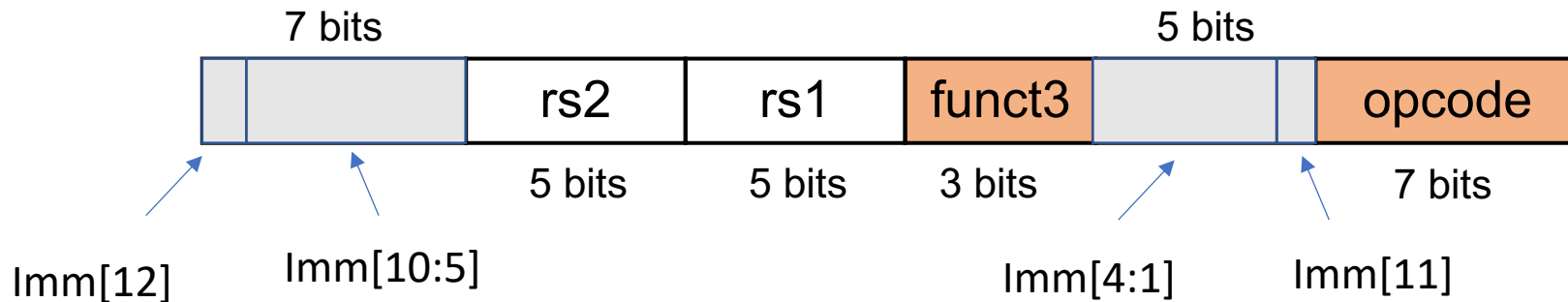Example SB-type instruction:

```
beq x5, x6, 100 // If (x5==x6) goto PC+2*100
```



- Immediate encodes a 12-bit signed integer offset.
- Branch address is $PC + \text{offset} * 2$


	opcode	funct3
beq	1100111	000
bne	1100111	001

Instruction Execution

- PC → fetch instruction from memory
- Register numbers → which register to read/write in register file
- Depending on instruction class, do the following:
 - Use ALU to calculate
 - Arithmetic result
 - Memory address for load/store
 - Branch comparison
 - Access data memory for load/store
 - PC ← either target address (branch) or PC + 4


ld x5, 40(x6)

x5 = Memory[x6+40]

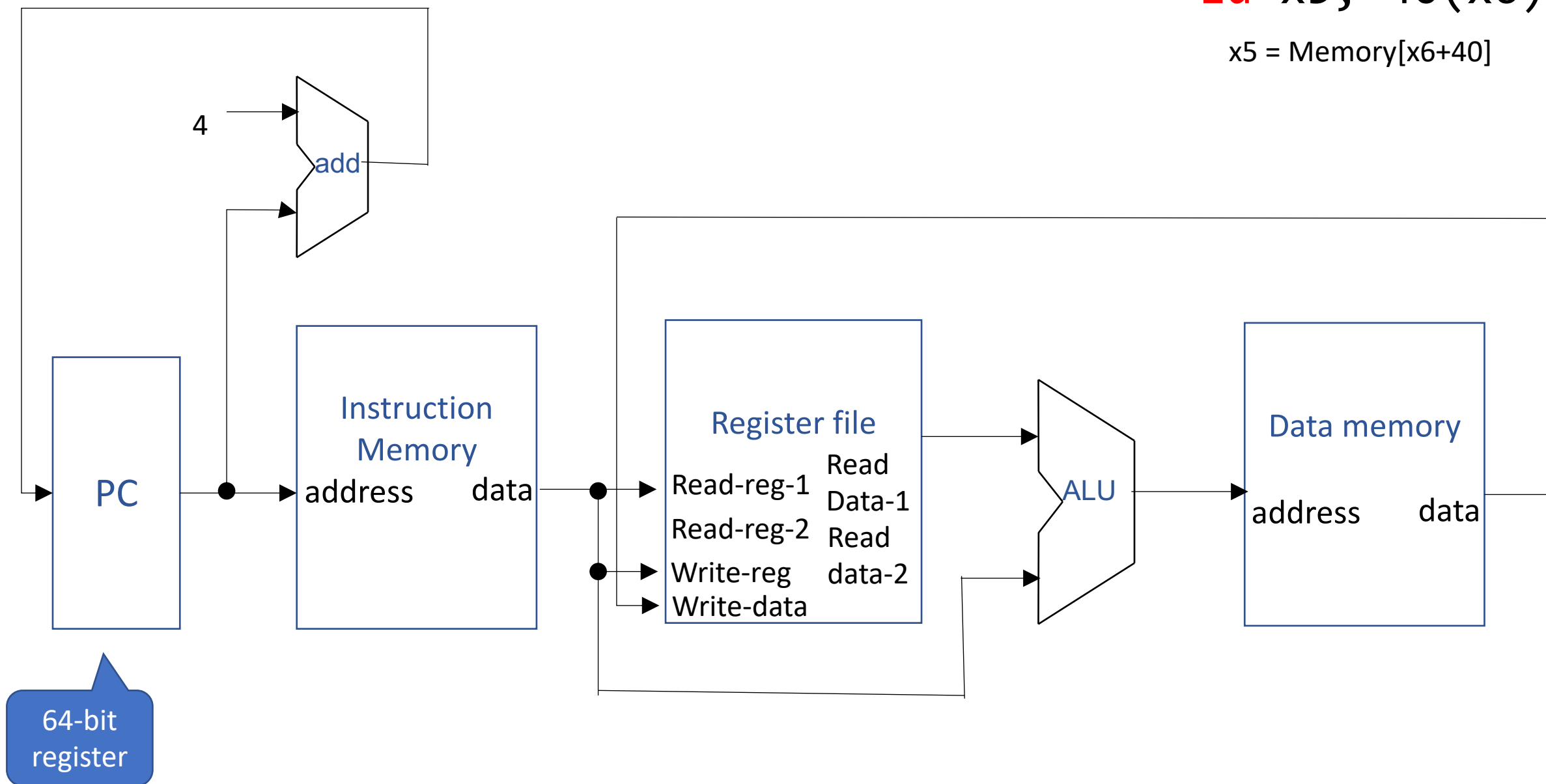


add x5, x6, x7

$$x5 = x6 + x7$$

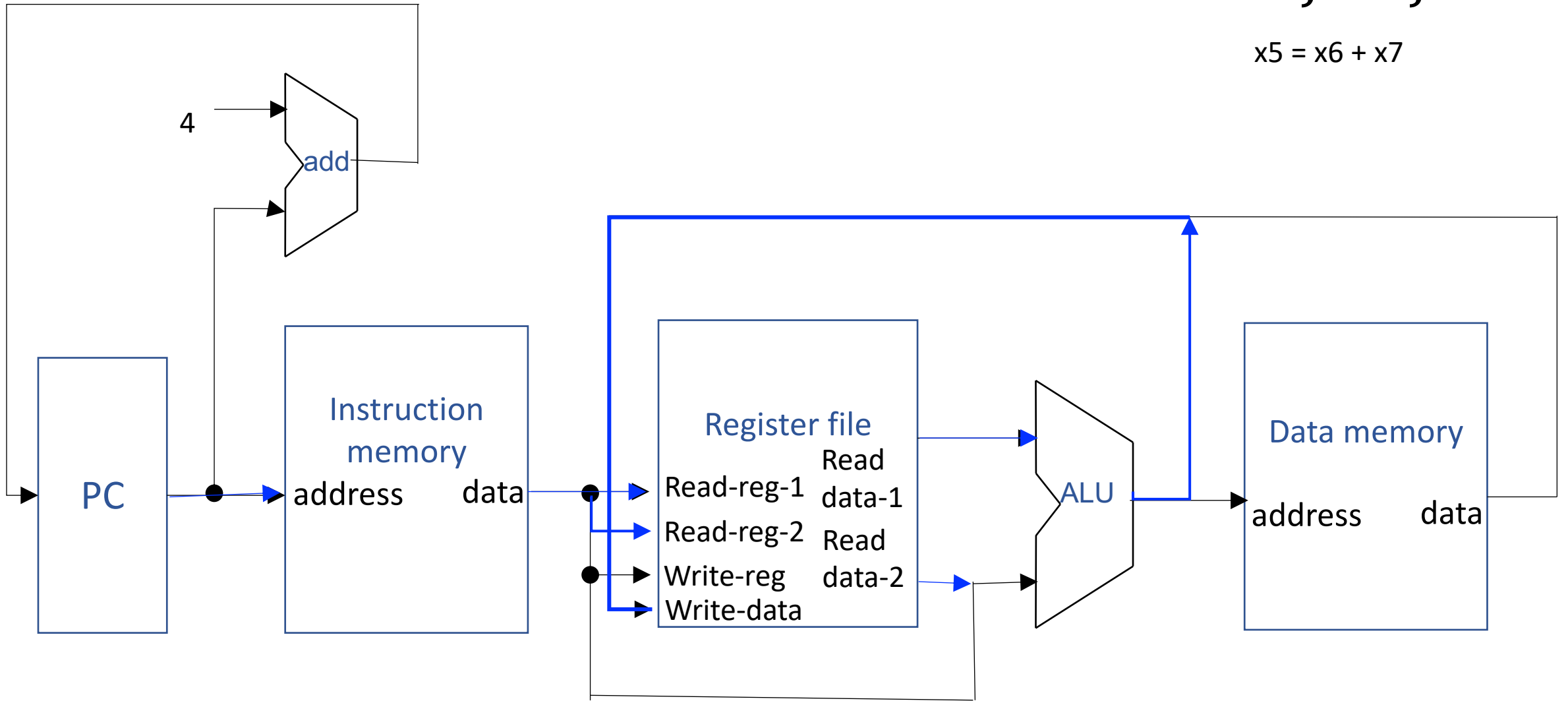


beq x5, x6, 100


If (x5==x6) goto PC+2*100

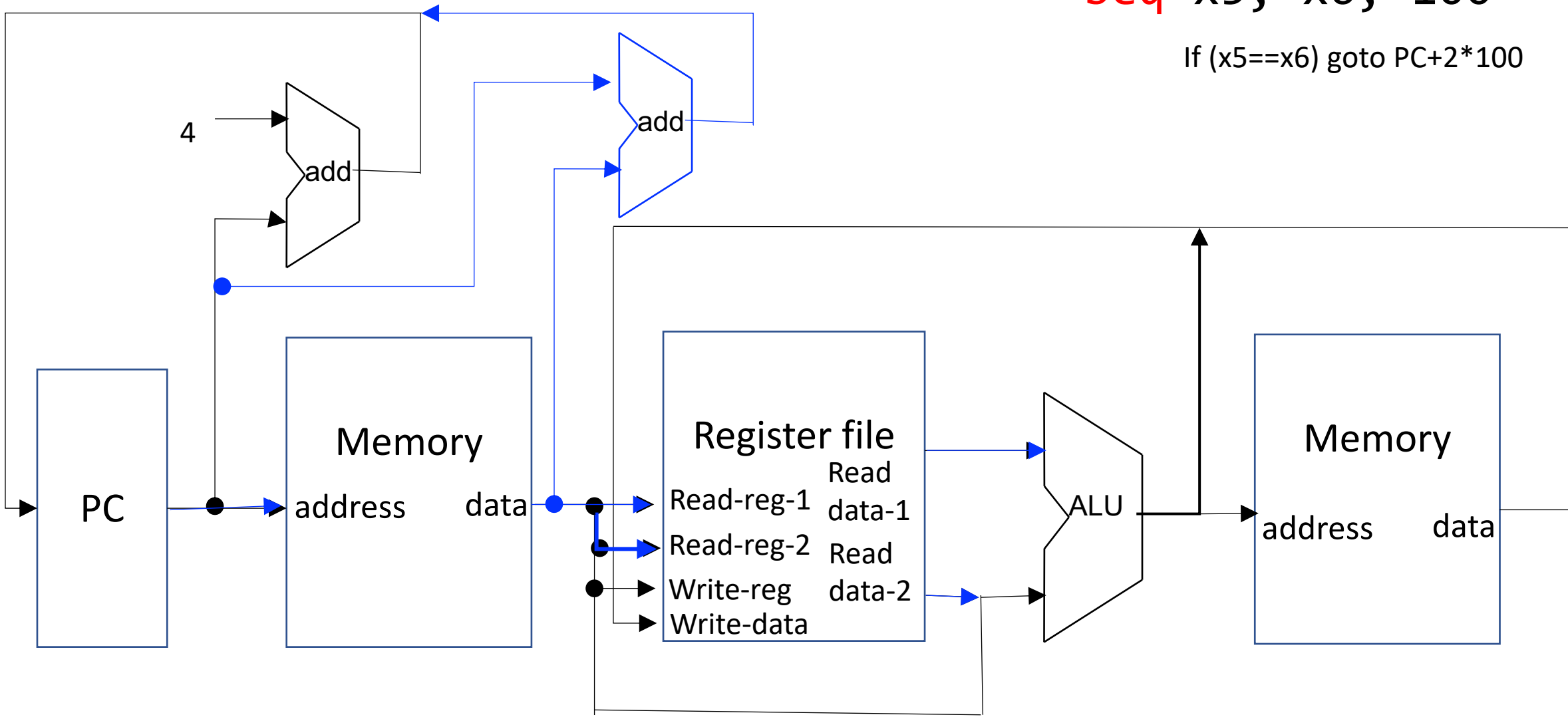

Instruction Execution

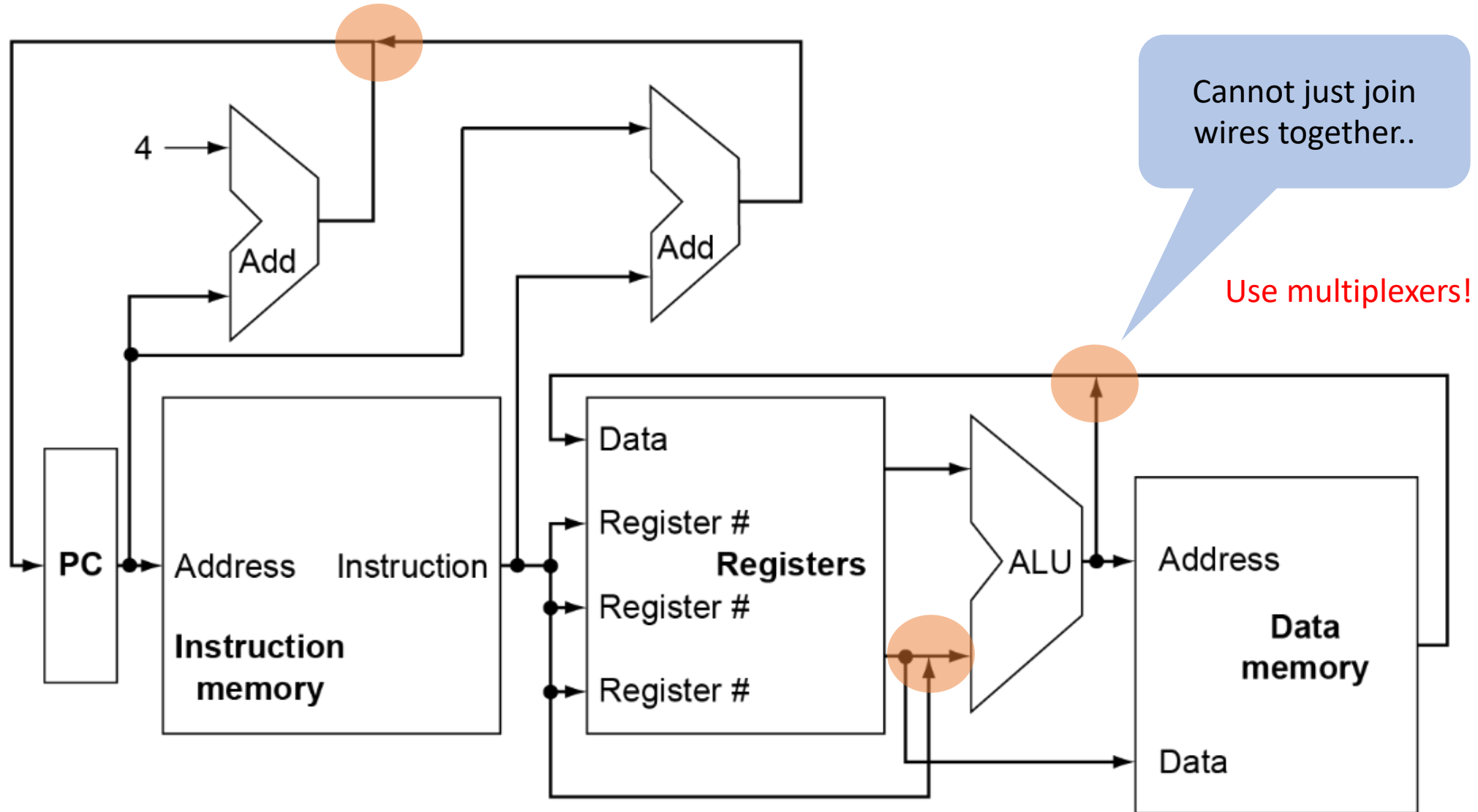


Data path vs. Control

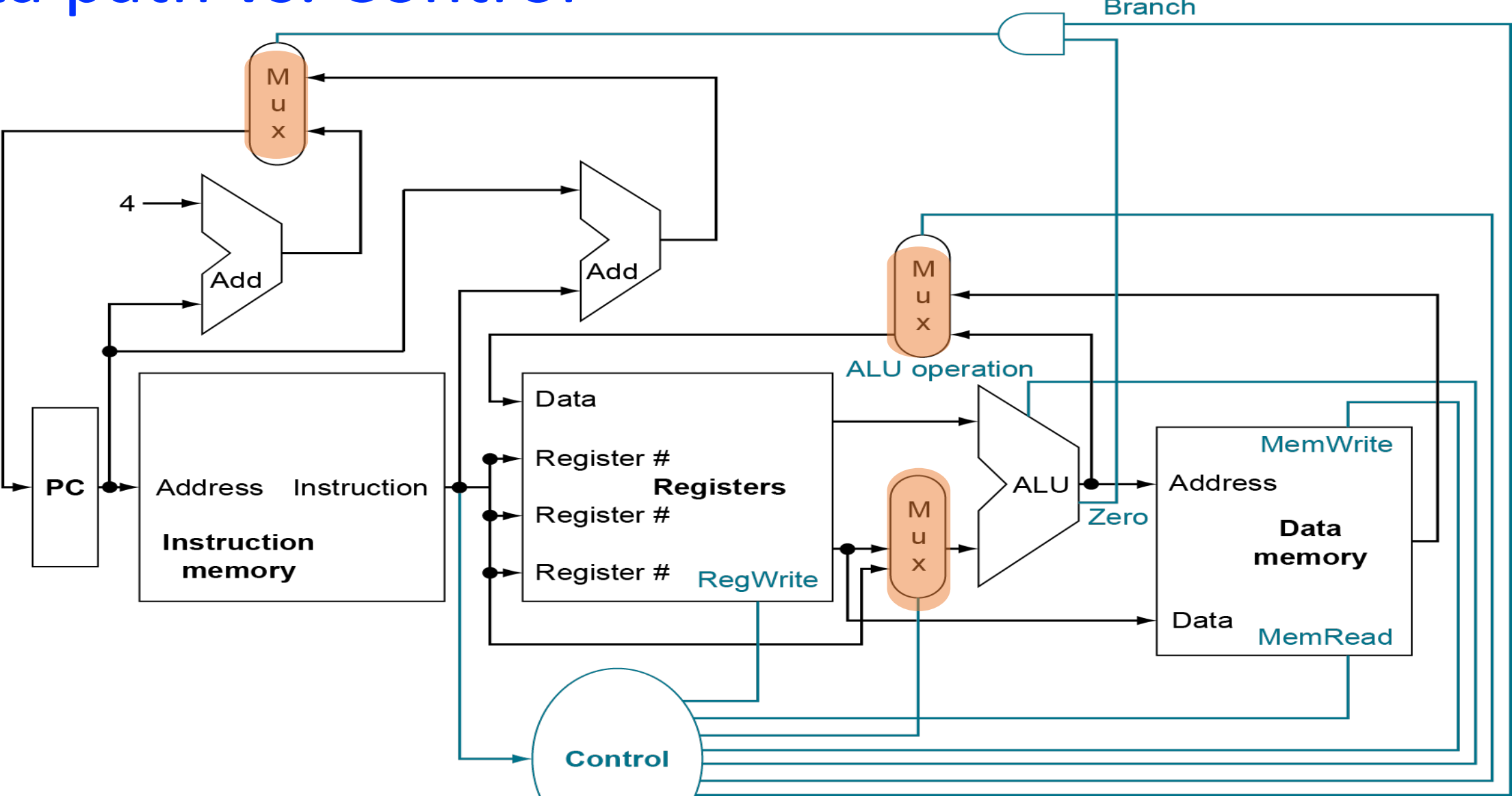


Building a Datapath

- Datapath: elements that process data and addresses in the CPU
 - Registers, ALUs, memories, ...
- We will refine our overview datapath design next...

R-Type/Load/Store Datapath

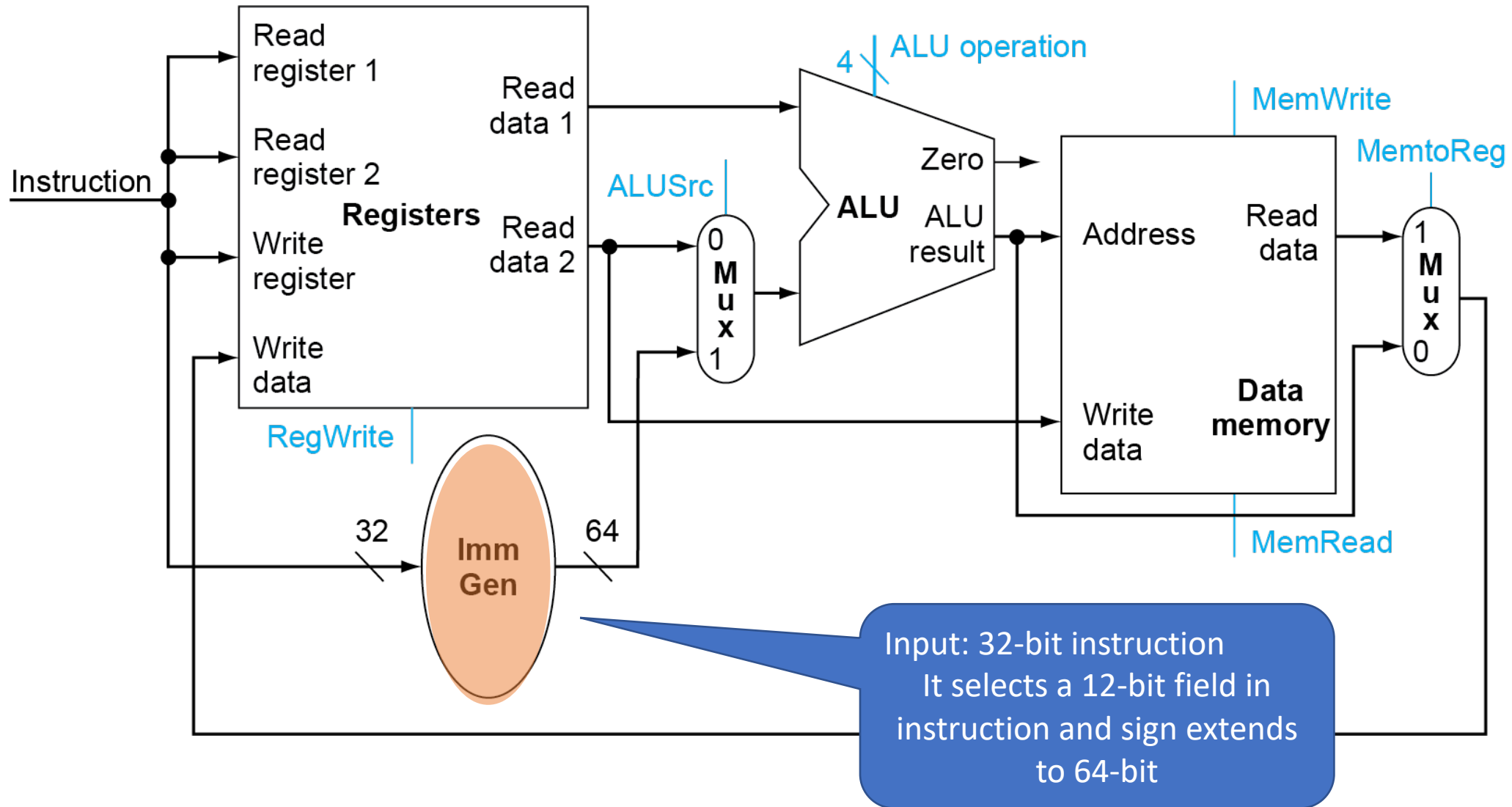

Full Datapath

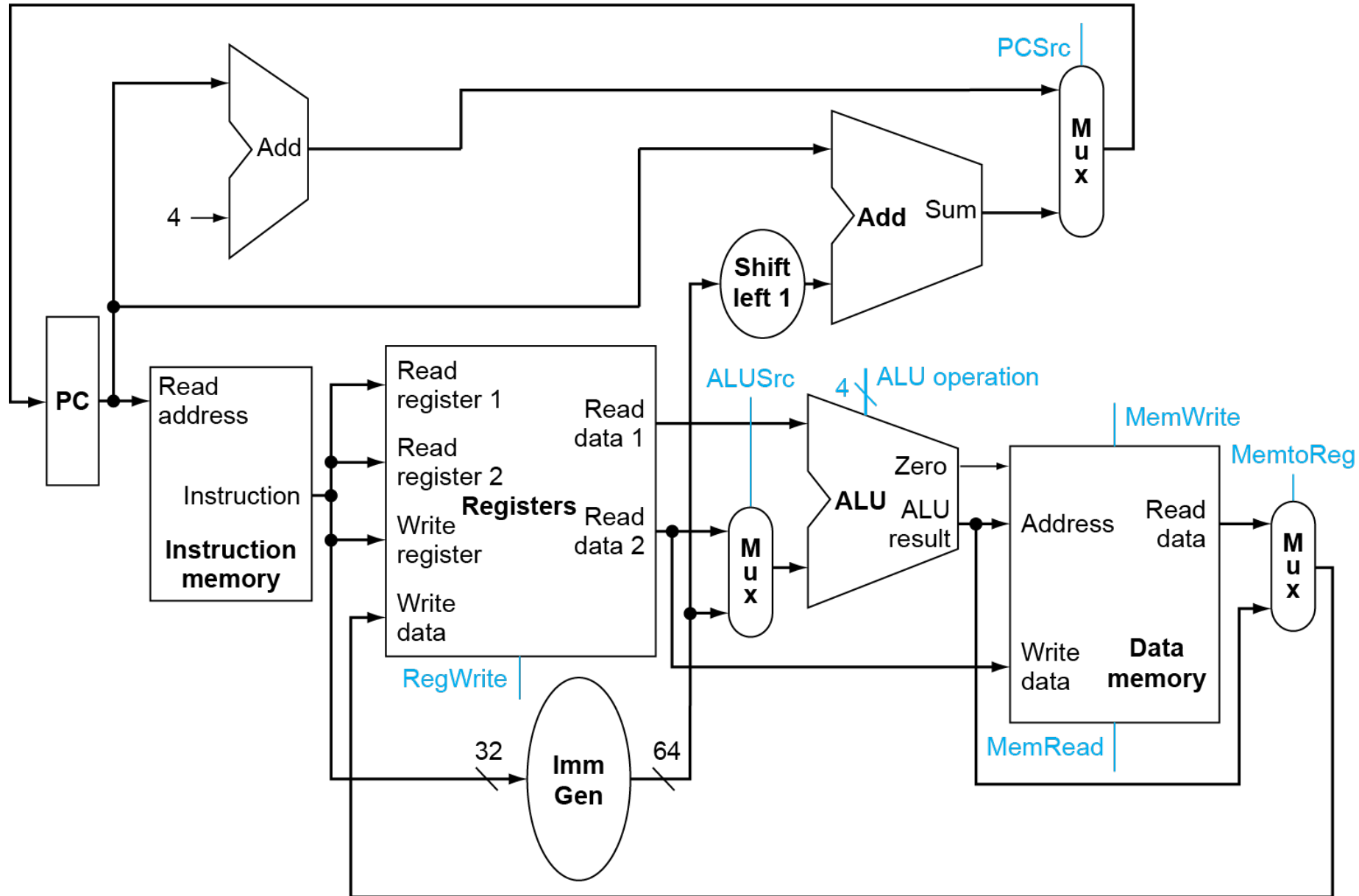

ALU Control

- ALU used for
 - Load/Store: F = add
 - Branch: F = subtract (for comparison)
 - R-type: F depends on opcode


ALU control lines	Function
0000	AND
0001	OR
0010	add
0110	subtract

ALU Control

- Assume a “Control” combinatorial logic that outputs 2-bit ALUOp derived from opcode
- Build an “ALU Control” combinatorial logic to output ALU control


opcode	ALU Op	Operation	func7	func3	ALU function	ALU control
ld	00	load register	xxxxxxx	xxx	add	0010
sd	00	store register	xxxxxxx	xxx	add	0010
beq	01	branch on equal	xxxxxxx	xxx	subtract	0110
R-type	10	add	000000	000	add	0010
		subtract	010000	000	subtract	0110
		AND	000000	111	AND	0000
		OR	000000	110	OR	0001

Datapath With Control

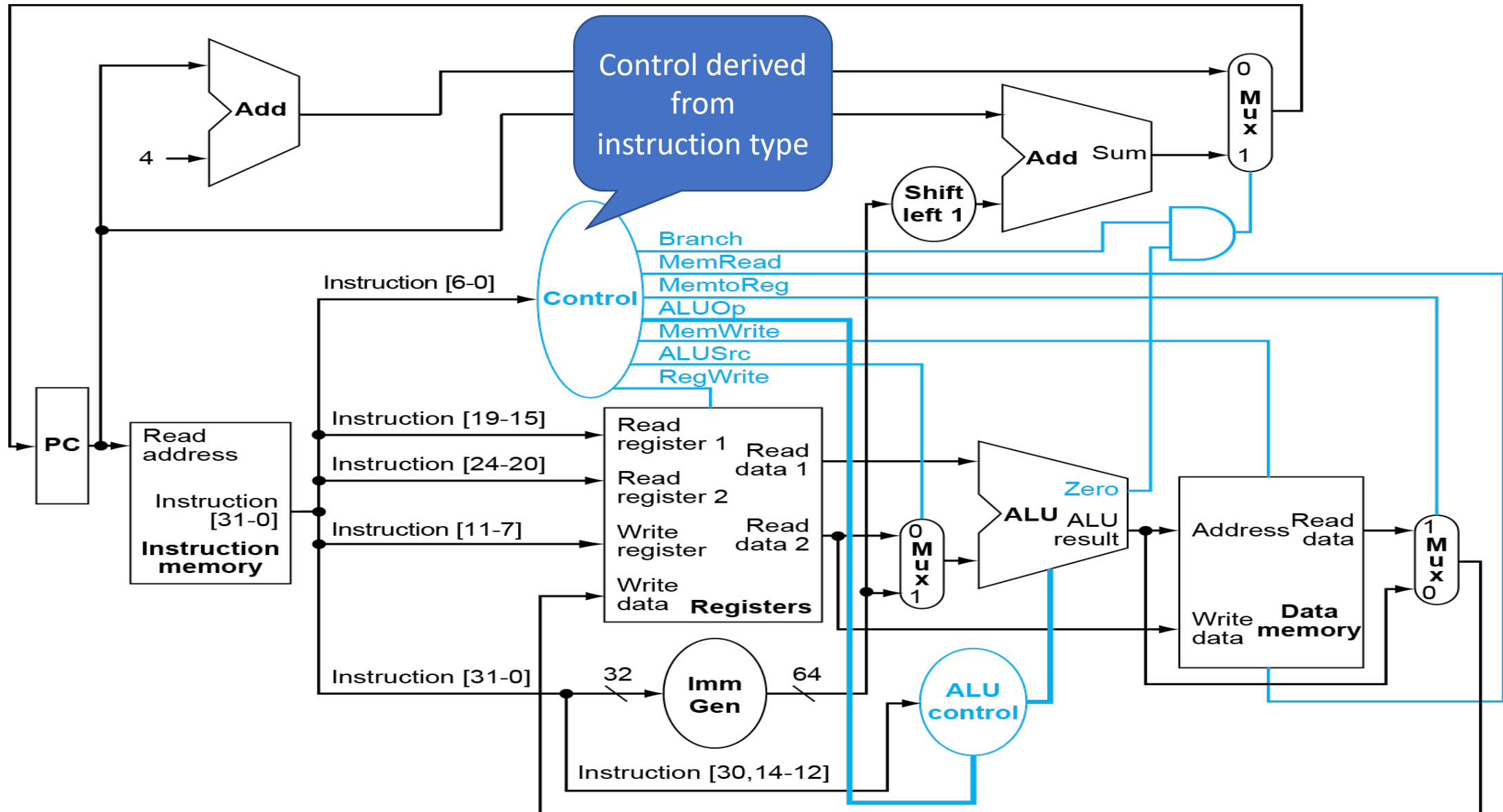

add x5, x6, x7


R-Type Inst

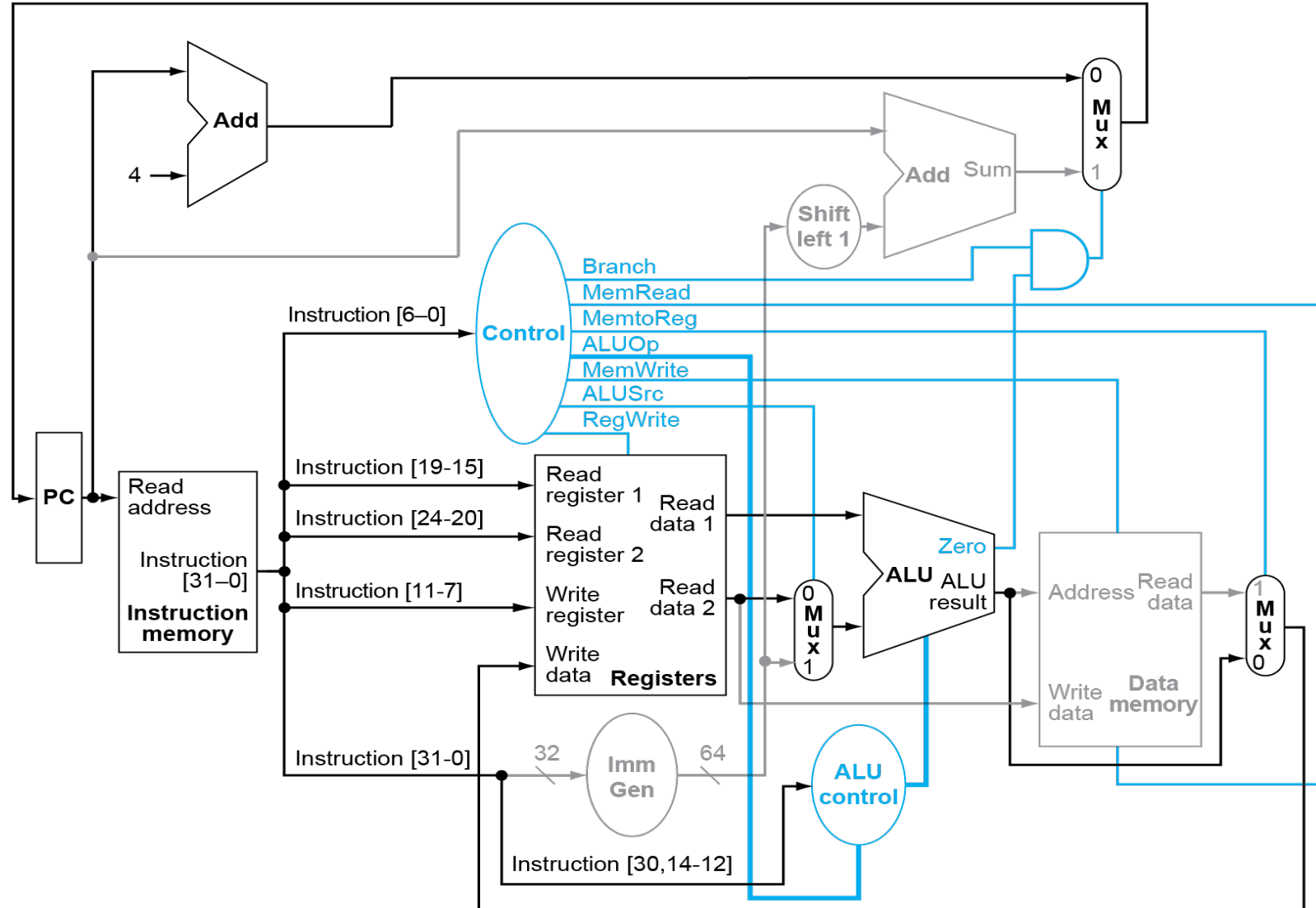

ld x5, 40(x6)


Load Inst

immediate	rs1	funct3	rd	opcode
-----------	-----	--------	----	--------

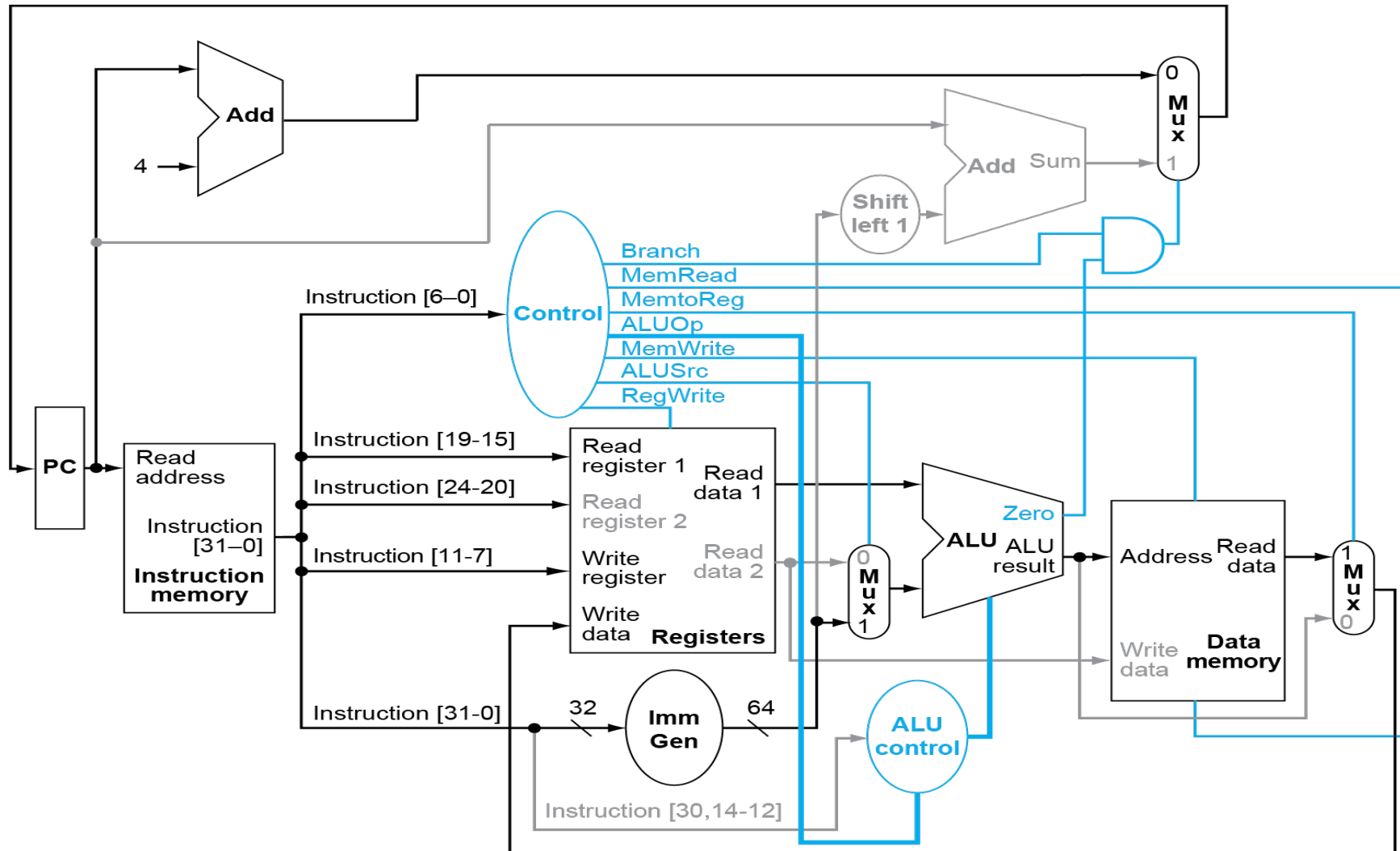

BEQ Instruction

beq x5, x6, 100

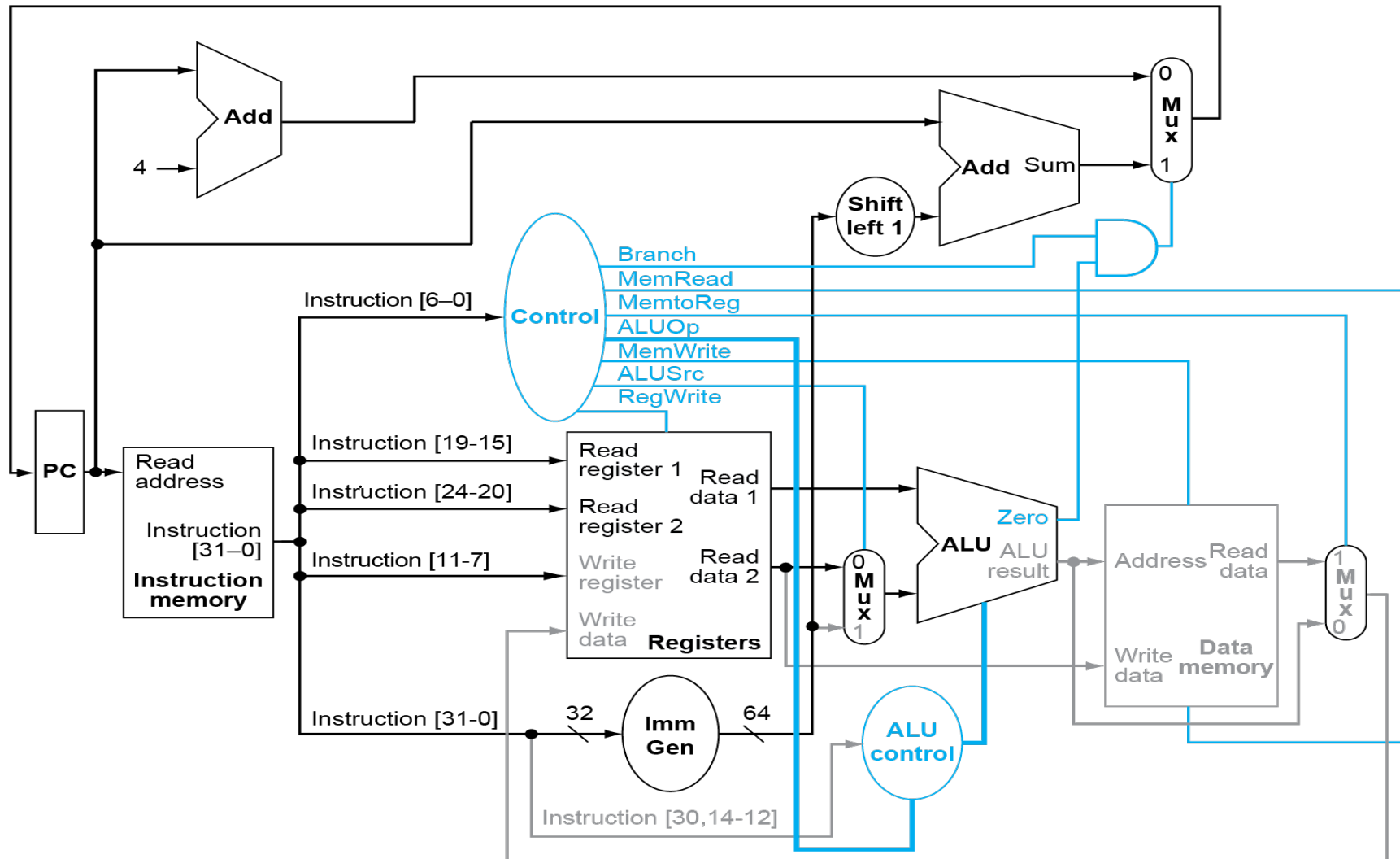

Performance Issues

- Longest delay determines clock period
 - Critical path: load instruction
 - Instruction memory → register file → ALU → data memory → register file
- Not feasible to vary clock period for different instructions
- Next lectures: We will improve performance by pipelining